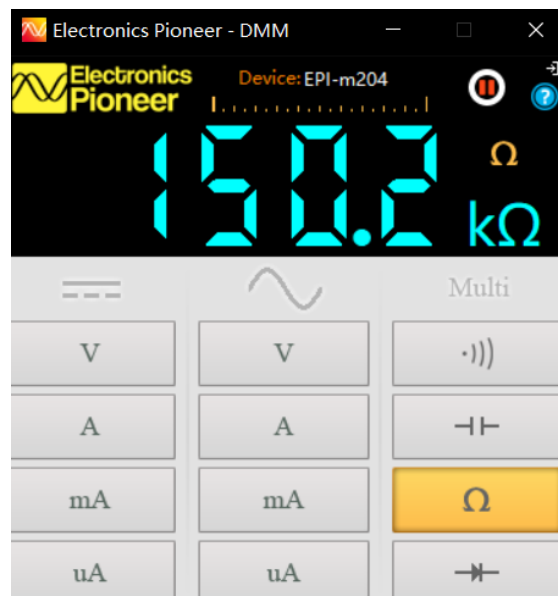


Quiz



易弘睿 20186103


庄研 20186105

1. Firstly, we use the Multimeter to measure the box , and we get a readable data: 150.2 k Ω , which means the box is a RC parallel connection of capacitor and resistor, and the resistance of the resistor is 150.2k Ω .




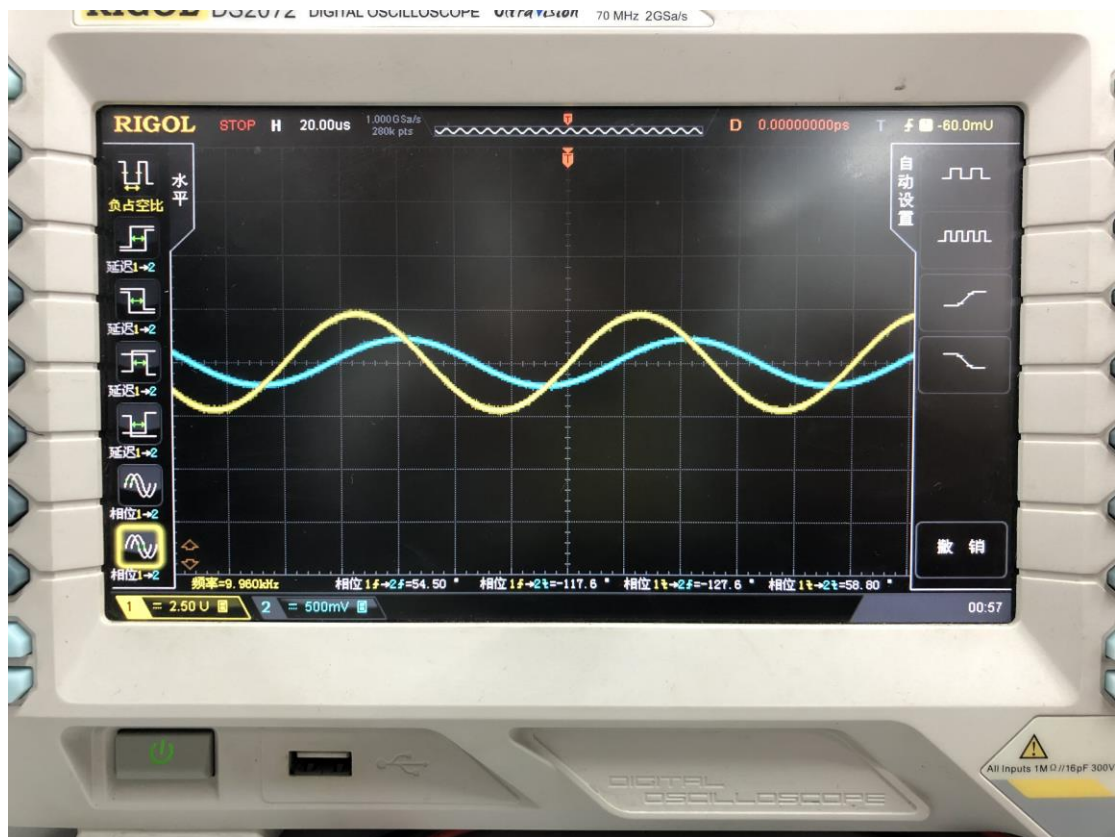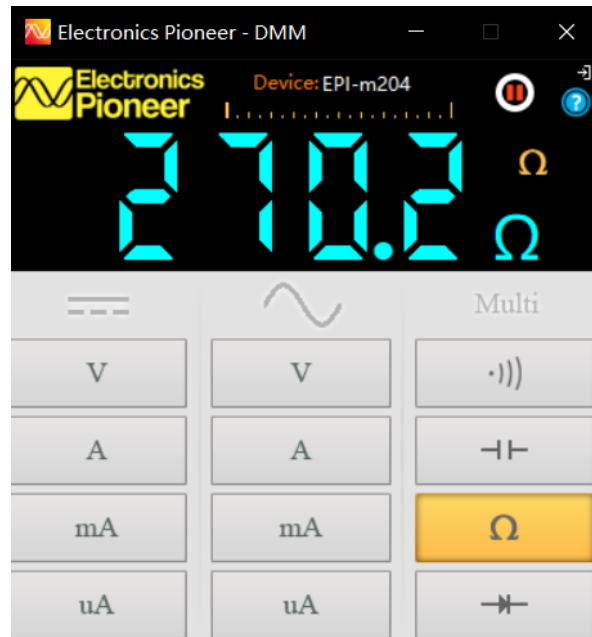2. Secondly, we observe the waveform with an oscilloscope. We choose a resistor whose resistance is 270.2k Ω , and make a series of it with the box. Then we give a HSS whose frequency is 10.000k Hz and the amplitude is 1.0k mVPP. The phase of voltage and current have phase difference, which is 58.8° so it is the RC parallel circuit.



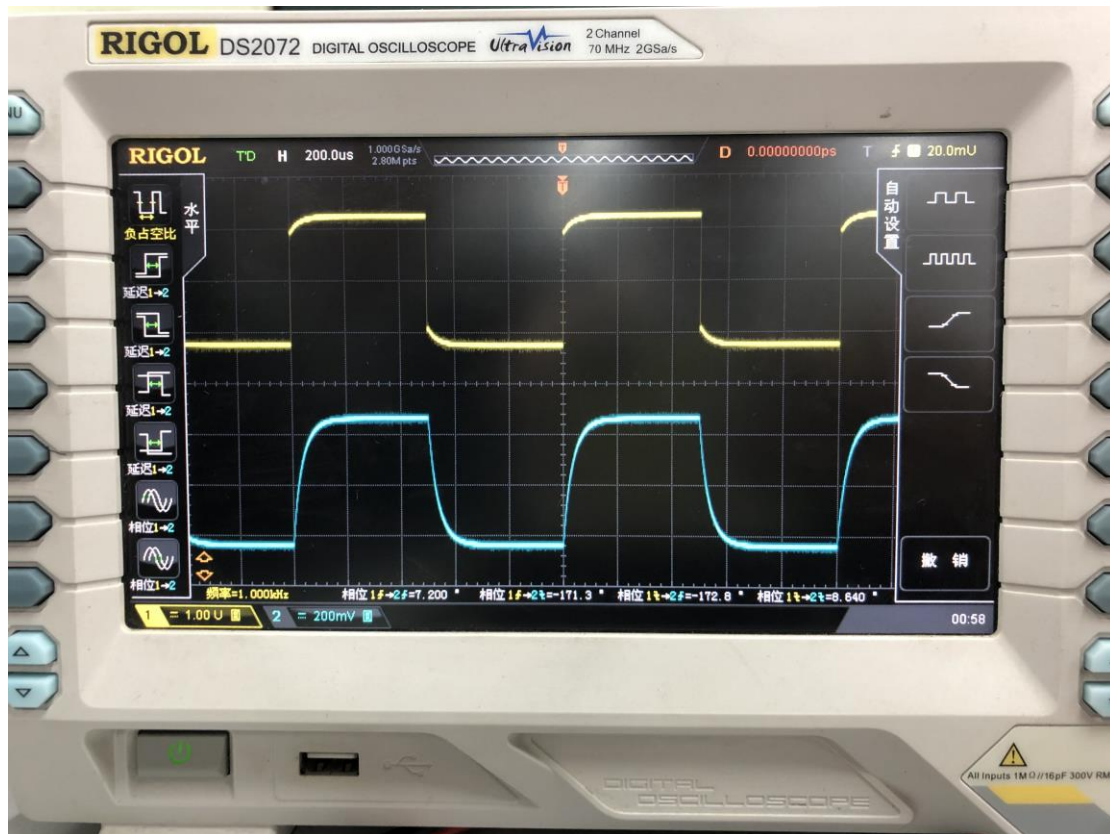

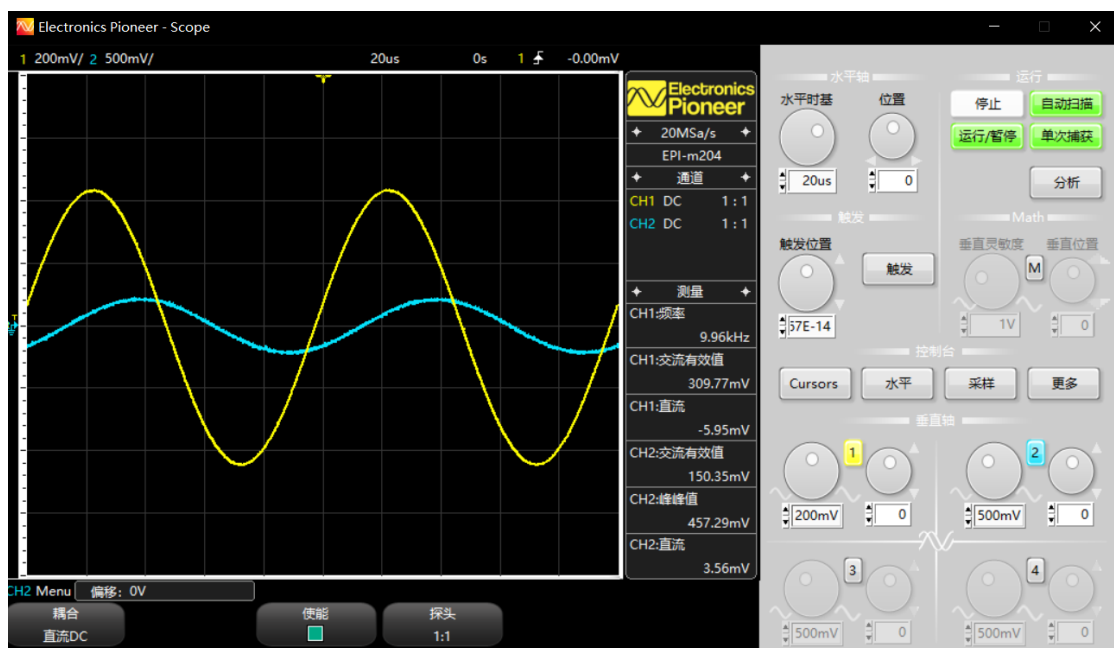- Thirdly, we use the equation to calculate the capacitance, and it is 0.1 μ F.



4. Finally, we use Multisim to check if our result is correct. The phase difference is $1/6$ cycle, so it is approximately, 60° . This demonstrate our calculation is right.

