

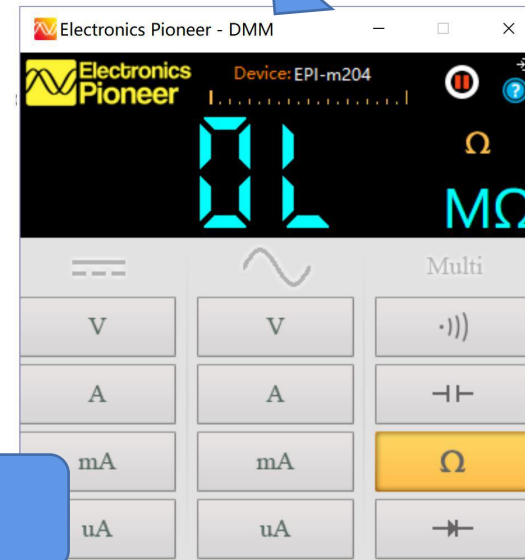
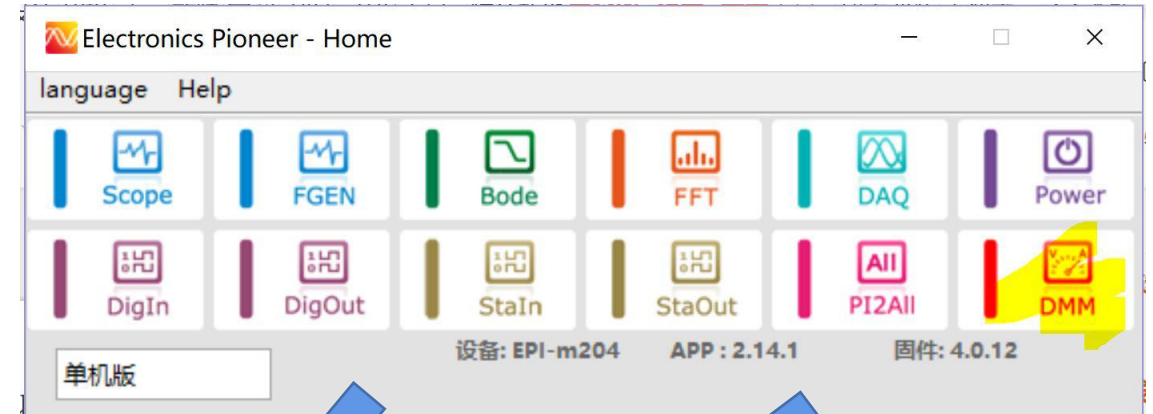


① Use the Multimeter to measure the black box

Electronics Pioneer APP

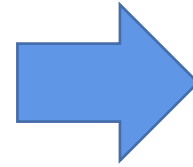

case A

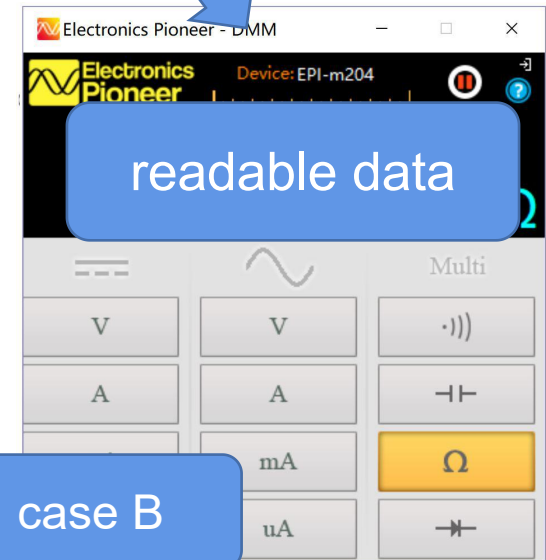

case B

- RC series connection
- Capacitance
- RC parallel connection
- Resistance



② Observe the waveform with an oscilloscope

=

case A

- RC series connection
- Capacitance

Series a
resistance ($\leq 200\Omega$)

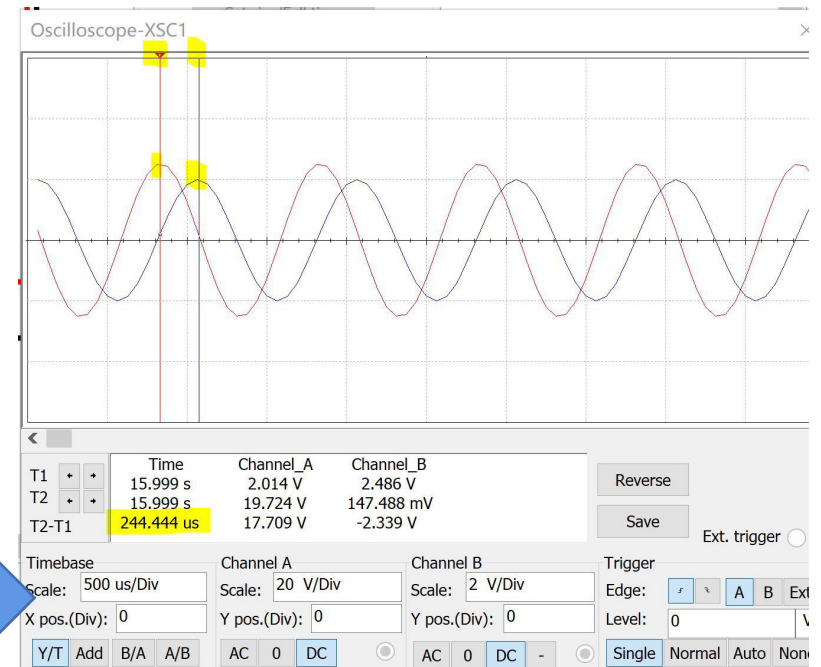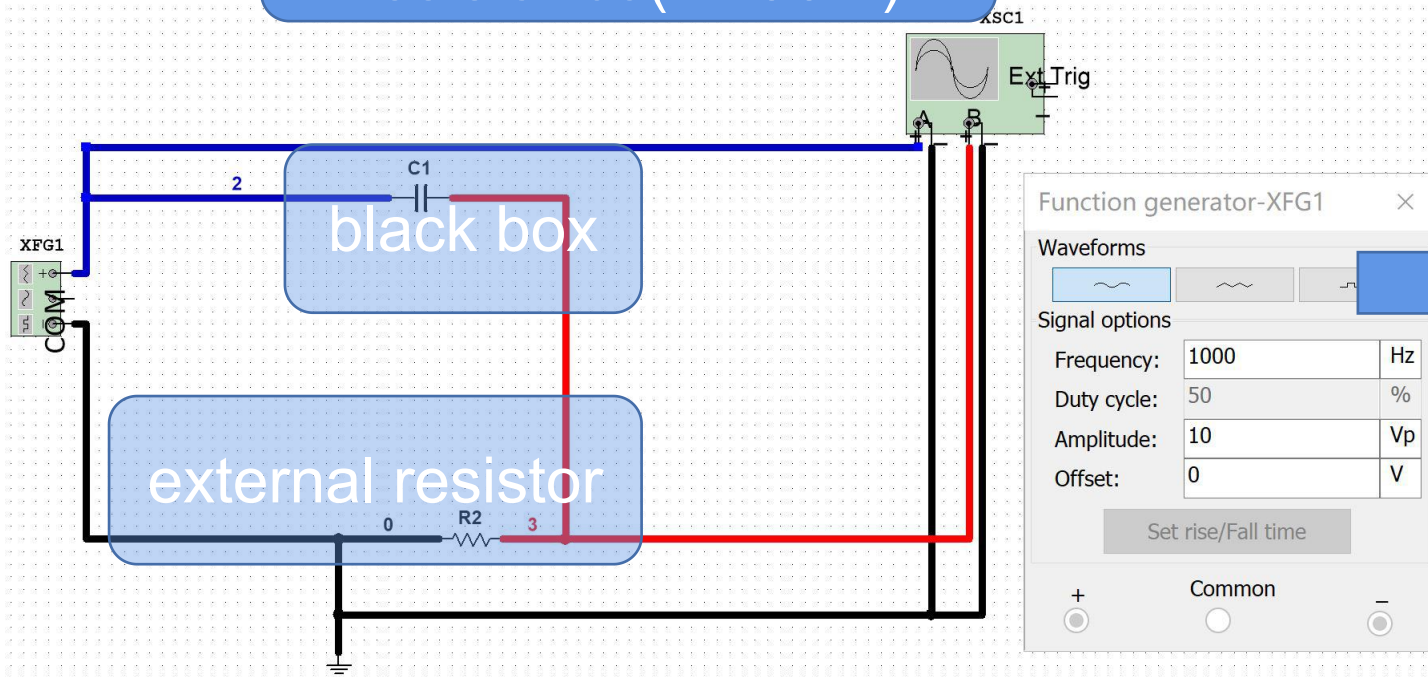

If the phase of the voltage and current is 90° , it is a capacitance.


② Observe the waveform with an oscilloscope

=

case A

- RC series connection
- Capacitance

③ Test the capacitance parameter

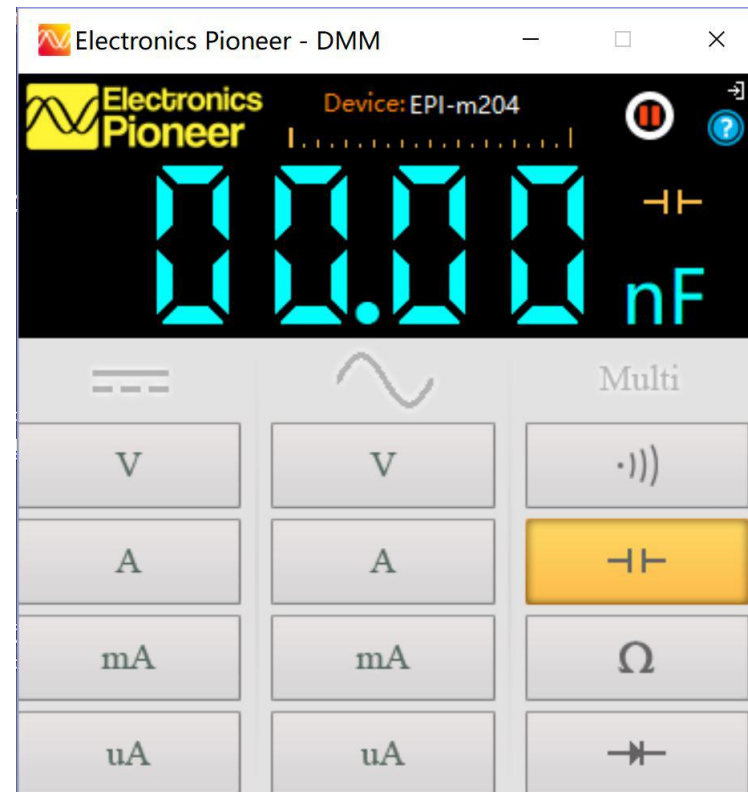



② Observe the waveform with an oscilloscope

=

case A

- RC series connection
- Capacitance

Series a
resistance($\leq 200\Omega$)

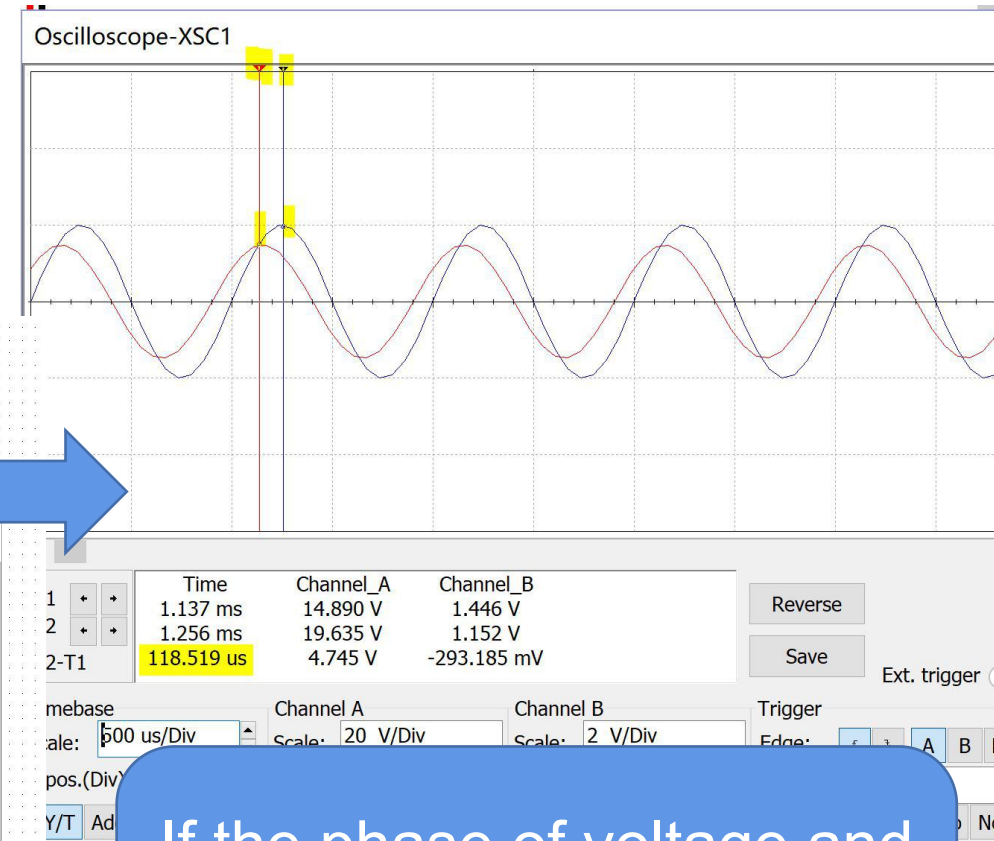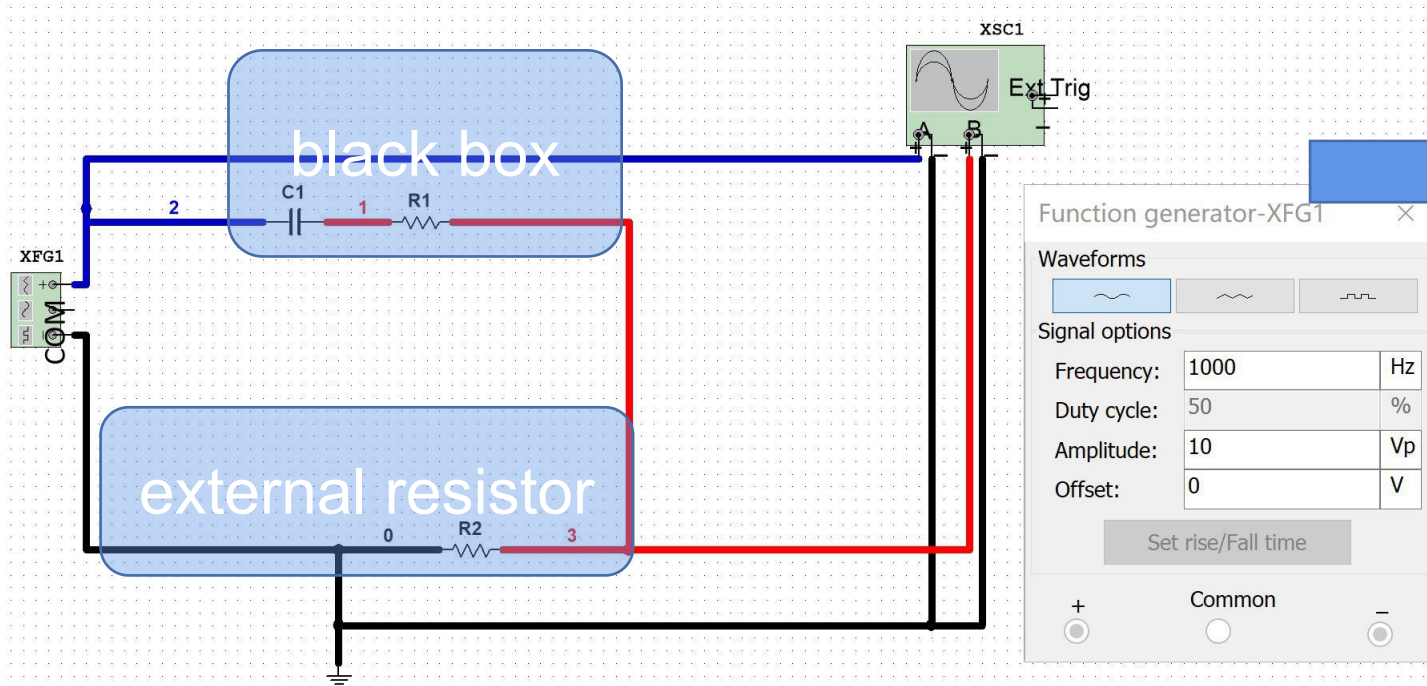

If the phase of voltage and current is **less than 90°** , it is the RC series circuit.



② Observe the waveform with an oscilloscope

=

case B

- RC parallel connection
- Resistance

Series a
resistance($\leq 200\Omega$)

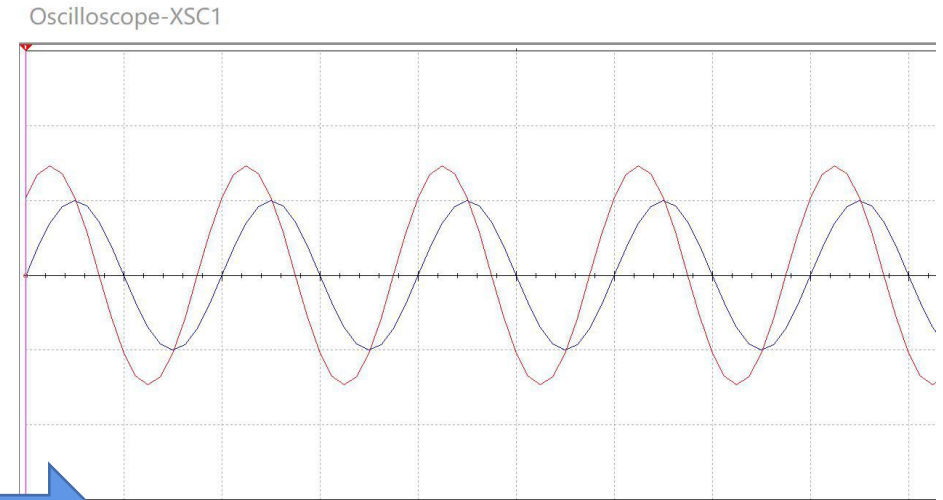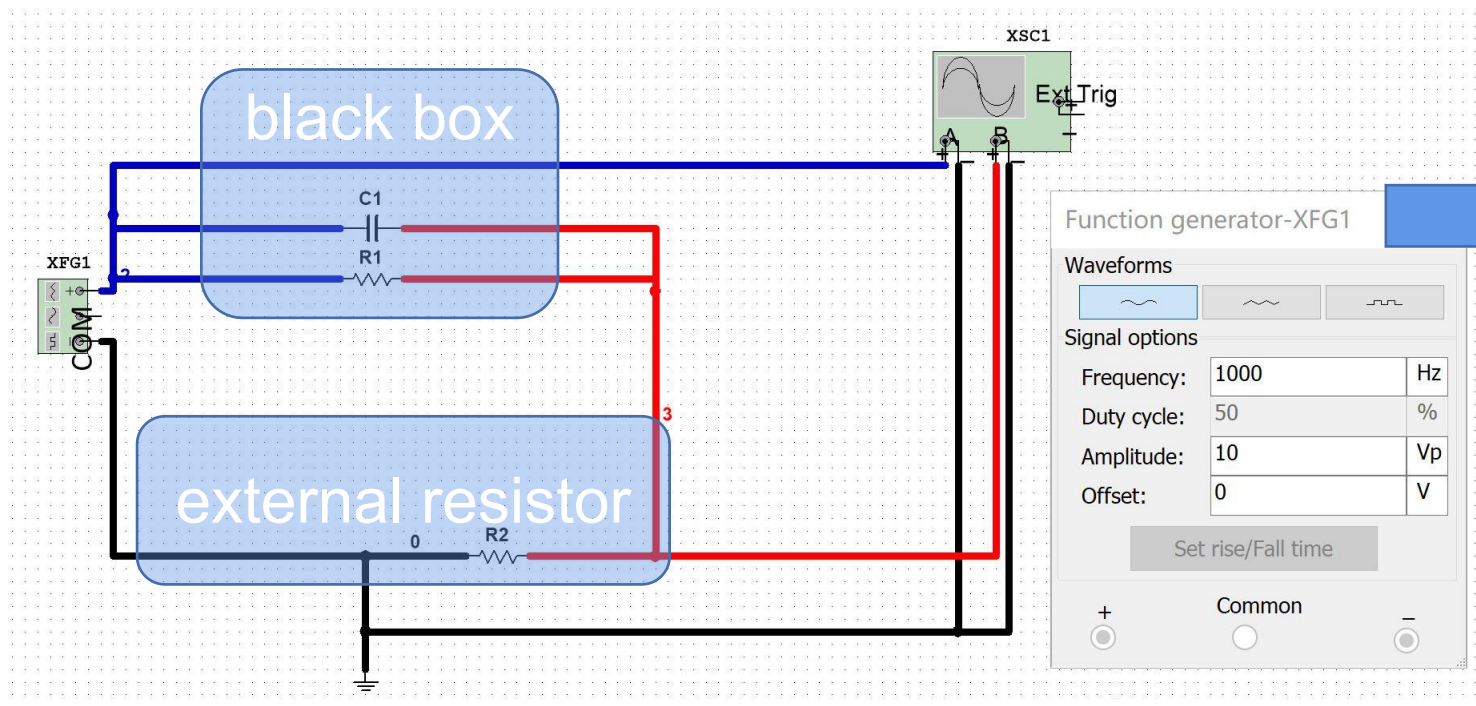

If voltage and current have phase difference, it is the RC parallel circuit.



② Observe the waveform with an oscilloscope

=

case B

- RC parallel connection
- Resistance

Series a
resistance($\leq 200\Omega$)

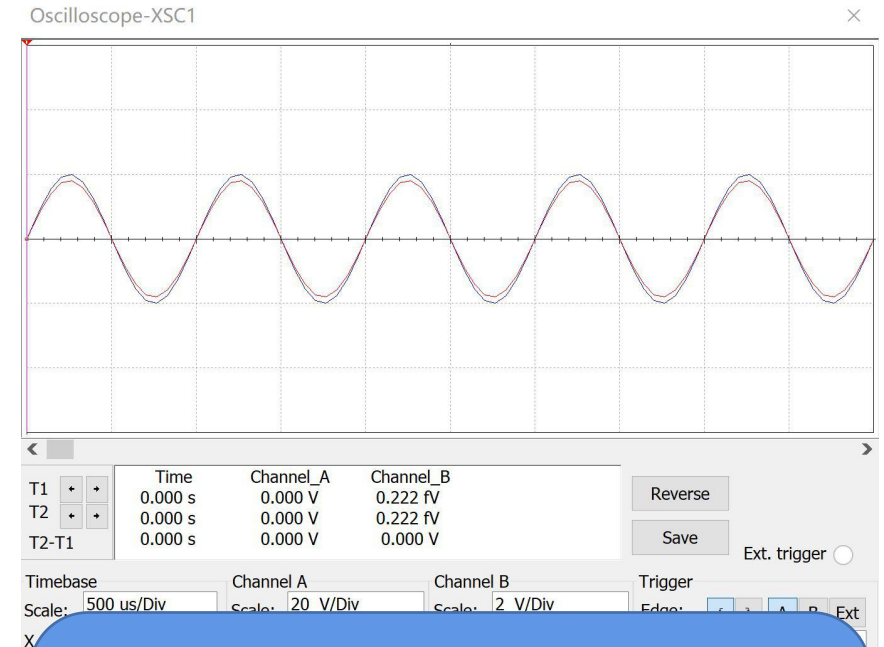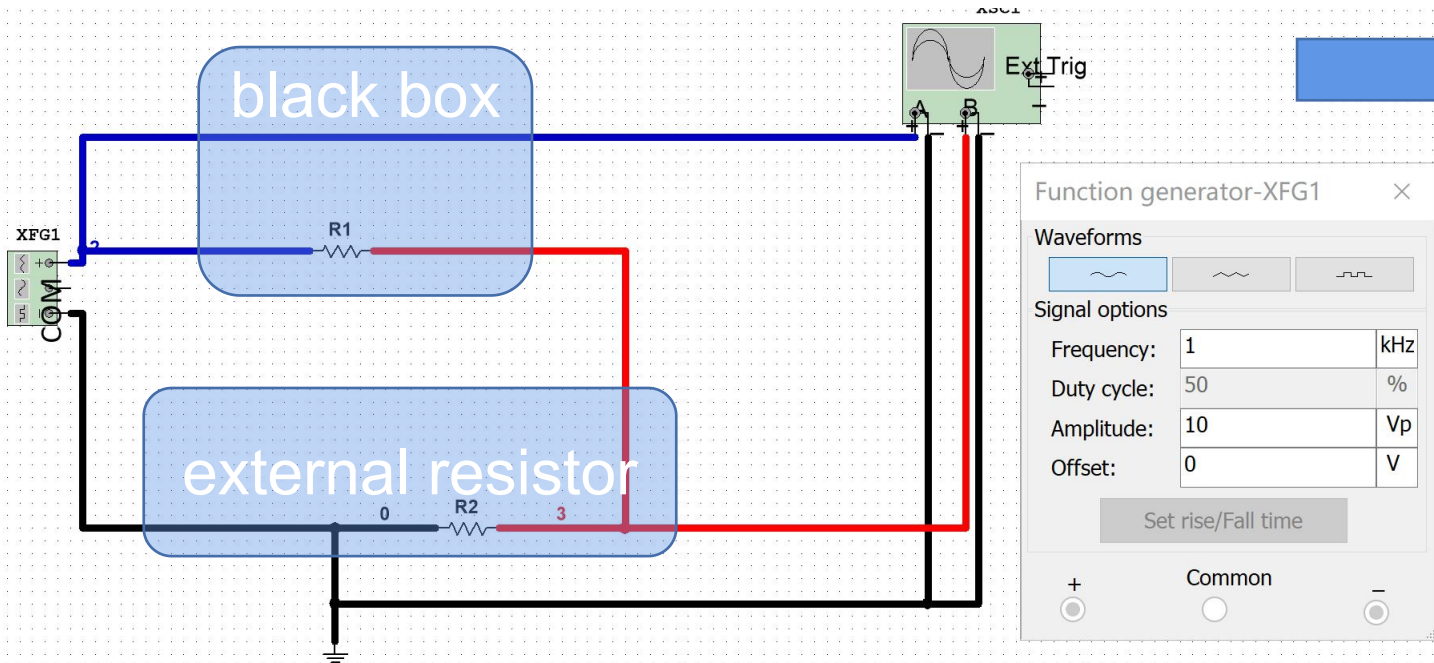

The voltage and current
are in phase and the
circuit is resistive.