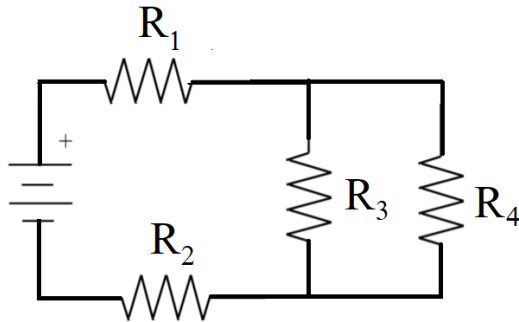


Review Assignment - Fall 2022

Problem #1: Determine the voltage across and current through R_4 in the circuit shown in the figure below for the given parameters.



$$V_{source} = 9V$$

$$R_1 = 22\Omega$$

$$R_2 = 33\Omega$$


$$R_3 = 100\Omega$$

$$R_4 = 47\Omega$$

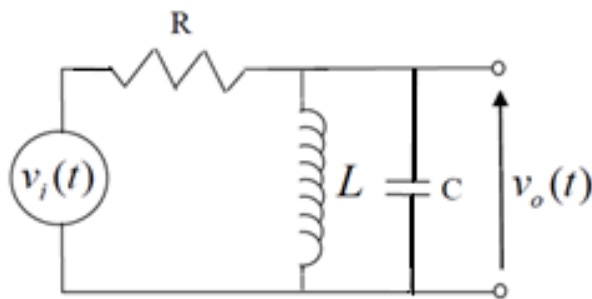Problem #2: The frequency response function (FRF) for the circuit shown below is:

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega L}{R - \omega^2 LC + j\omega L}$$

Using Matlab, plot the magnitude (in dB) & phase (in degrees) of the FRF for the given parameters.
Note: this should be on one figure using subplots; also use "semilogx" to plot frequency on a log scale



$$R = 50\Omega$$

$$L = 800 \text{ mH}$$

$$C = \mu F$$

$$0 \leq f \leq 100,000 \text{ Hz}$$

$$1 \text{ Hz intervals}$$

Review Assignment - Fall 2022

Problem #3: A vibrating system has the following parameters:

$$\begin{aligned}m &= 0.5 \text{ kg} \\k &= 975 \text{ N/cm} \\c &= 2.5 \text{ N*s/cm}\end{aligned}$$

Determine:

- the damped natural frequency (*in Hz*)
- the undamped natural frequency (*in Hz*)
- the damping ratio

[Ans: $\omega = 57.9\text{Hz}$, $\Omega = 70.3\text{Hz}$, $\zeta = 0.566$]


Problem #4: An unknown mass of m kg attached to the end of an unknown spring k has a natural frequency of 314 Hz. When a 1-kg mass is added to m , the natural frequency is lowered to 275 Hz.

Determine:

- the unknown mass m (in kg)
- the spring constant k (in MN/m)

[Ans: $m = 3.29 \text{ kg}$, $k = 12.8 \text{ MN/m}$]

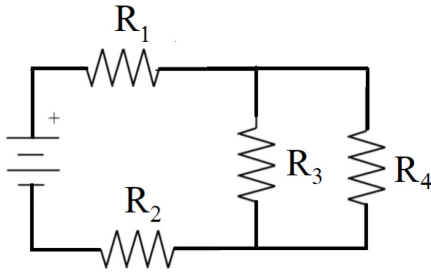Problem #1: Determine the voltage across and current through R_4 in the circuit shown in the figure below for the given parameters.



$$V_{source} = 9V$$

$$R_1 = 22\Omega$$

$$R_2 = 33\Omega$$

$$R_3 = 100\Omega$$

$$R_4 = 47\Omega$$

For R_3, R_4 :

$$R_{eq} = \frac{R_3 \cdot R_4}{R_3 + R_4} = \frac{100 \times 47}{100 + 47} = 31.97\Omega$$

$$V_4 = V_{source} \cdot \frac{R_{eq}}{R_1 + R_2 + R_{eq}} = 9 \times \frac{31.97}{22 + 33 + 31.97} = 3.31V$$

$$I_4 = \frac{V_4}{R_4} = \frac{3.31}{47} = 0.0704A = 70.4mA$$

Problem #3: A vibrating system has the following parameters:

$$m = 0.5 \text{ kg}$$

$$k = 975 \text{ N/cm}$$

$$c = 2.5 \text{ N*s/cm}$$

Determine:

- the damped natural frequency (*in Hz*)
- the undamped natural frequency (*in Hz*)
- the damping ratio

[Ans: $\omega = 57.9\text{Hz}$, $\Omega = 70.3\text{Hz}$, $\zeta = 0.566$]

$$(a) \omega_r = \sqrt{\frac{k}{m} - \left(\frac{c}{2m}\right)^2} = \sqrt{\frac{97500}{0.5} - \left(\frac{250}{2 \times 0.5}\right)^2} = 364 \text{ rad/s or } 57.9 \text{ Hz}$$

$$(b) \Omega_r = \sqrt{\frac{k}{m}} = \sqrt{\frac{97500}{0.5}} = 441.5 \text{ rad/s or } 70.3 \text{ Hz}$$

$$(c) \zeta = \frac{c}{2\sqrt{mk}} = \frac{250}{2\sqrt{0.5 \times 97500}} = 0.566$$

Problem #4: An unknown mass of m kg attached to the end of an unknown spring k has a natural frequency of 314 Hz. When a 1-kg mass is added to m , the natural frequency is lowered to 275 Hz.

Determine:

- the unknown mass m (in kg)
- the spring constant k (in MN/m)

[Ans: $m = 3.29$ kg, $k = 12.8$ MN/m]

$$\omega_1 = 314 \text{ Hz} \quad \omega_2 = 275 \text{ Hz}$$

$$\text{We have } \begin{cases} \omega_1 = \sqrt{\frac{k}{m}} = 314 \text{ Hz} \\ \omega_2 = \sqrt{\frac{k}{m+1}} = 275 \text{ Hz} \end{cases}$$


$$\text{By calculation: } \begin{cases} m = 3.29 \text{ kg} \\ k = 12.81 \times 10^6 \text{ N/m} \end{cases}$$

Problem #2: The frequency response function (FRF) for the circuit shown below is:

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega L}{R - \omega^2 LC + j\omega L}$$

Using Matlab, plot the magnitude (in dB) & phase (in degrees) of the FRF for the given parameters.

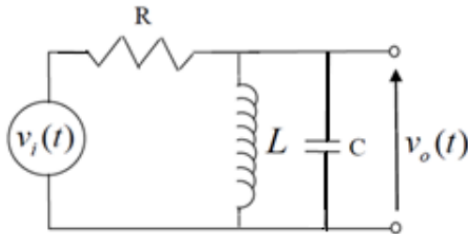Note: this should be on one figure using subplots; also use "semilogx" to plot frequency on a log scale



$$R = 50\Omega$$

$$L = 800\text{ mH}$$

$$C = \mu\text{F}$$

$$0 \leq f \leq 100,000\text{ Hz}$$

$$1\text{ Hz intervals}$$

Code:

```
%% HW1
```

```
% Name: Hongrui Yi
```

```
% Content: Q2 HW1
```

```
%% Initialization
```

```
close all; clear; clc;
```

```
%% Set parameter
```

```
R = 60; % Set the value for the  
resistance
```

```
L = 800*10^(-3); % Set the value for the  
inductor
```

```
C = 33*10^(-6); % Set the value for the  
capacitor
```

```
f = 0:1:100000; % Set the value for the  
frequency
```

```

H = zeros(size(f)); % Create a matrix for the
frequency response function (FRF)

%% Calculation

for i = 1:length(f)
H(i) = (1i*2*pi*f(i)*L)/(R-
(2*pi)^2*(f(i).^2)*L*C+1i*2*pi*f(i)*L); %
Calculate the FRF
end

%% Result

figure % Make the graph
subplot(2,1,1) % Create the first subplot of 2
rows, 1 column
semilogx(f,2*abs(H)) % Make the frequency in a
log scale
xlabel(['$ f\;\mathrm{[Hz]}$'], 'interpreter', 'latex') % Create a label
for x
ylabel(['$ magnitude\;\mathrm{[dB]}$'], 'interpreter', 'latex') % Create a label
for y
grid on % Open the grid
subplot(2,1,2) % Create the second subplot of

```

```

2 rows, 1 colum

semilogx(f,rad2deg(angle(H))) % Make the
frequency in a log scale

xlabel(['$ f\;;\mathrm{[Hz]}$'], 'interpreter', 'latex') % Create a label
for x

ylabel(['$ phase\;;\mathrm{[dB]}$'], 'interpreter', 'latex') % Create a label
for y

grid on % Open the grid

```

Graph:

