

Student ID:

Student name:

Electrical Engineering Lab

Quiz

- Component (Multiple topics)

☐ Resistor

☐ Capacitance

☐ Inductance

- Component parameters

Resistor: _____

Capacitance: _____

Inductance: _____

- Connection

☐ Series connection

☐ Parallel connection

- Experimental analysis

(It is only the **process of analysis** that is filled in the experiment analysis, and the **results of measurements and simulations** were uploaded to the *Discussion Area of Rain Classroom* in the form of pictures)